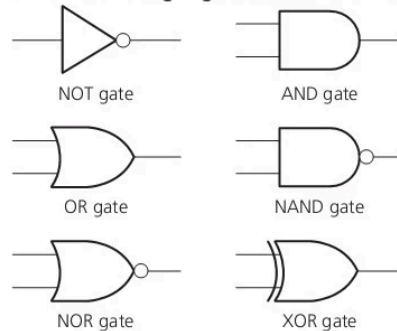


10.1.1 Logic gate symbols

Six different logic gates will be considered in this chapter:



▲ **Figure 10.1** Logic gate symbols

Truth tables

Truth tables are used to trace the output from a logic gate or logic circuit. The NOT gate is the only logic gate with one input; the other five gates have two inputs (see Figure 10.1).

Although each logic gate can only have one or two inputs, the number of inputs to a logic circuit can be more than 2; for example, three inputs give a possible 2^3 (=8) binary combinations. And for four inputs, the number of possible binary combinations is 2^4 (=16). It is clear that the number of possible binary combinations is a multiple of the number 2 in every case. The possible inputs in a truth table can be summarised as shown in Table 10.1.

▼ **Table 10.1** All possible inputs for truth tables with two, three and four inputs

Inputs	
A	B
0	0
0	1
1	0
1	1

Inputs		
A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


Inputs			
A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

10 BOOLEAN LOGIC

As we can see, a truth table will also list the output for every possible combination of inputs.

10.2 The function of the six logic gates

10.2.1 NOT gate

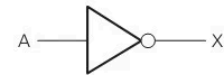

▲ Figure 10.2

Description:	Truth table:	How to write this:								
<p>The output, X, is 1 if:</p> <p>the input, A, is 0</p>	<p>▼ Table 10.2</p> <table><tr><th>Input</th><th>Output</th></tr><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	Input	Output	A	X	0	1	1	0	<p>X = NOT A (logic notation)</p> <p>X = \overline{A} (Boolean algebra)</p>
Input	Output									
A	X									
0	1									
1	0									

Note the use of Boolean algebra to represent logic gates. This is optional at IGCSE but many students may prefer to use this notation (see NOTE later).

10.2.2 AND gate



▲ Figure 10.3

Description:	Truth table:	How to write this:																		
The output, X, is 1 if: both inputs, A and B, are 1	<div>▼ Table 10.3</div> <table><tr><th colspan="2">Inputs</th><th>Outputs</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	Inputs		Outputs	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1	$X = A \text{ AND } B$ (logic notation) $X = A \cdot B$ (Boolean algebra)
Inputs		Outputs																		
A	B	X																		
0	0	0																		
0	1	0																		
1	0	0																		
1	1	1																		

10.2.3 OR gate



▲ Figure 10.4

Description:	Truth table:	How to write this:																		
The output, X, is 1 if: either input, A or B, or both, are 1	<div>▼ Table 10.4</div> <table><tr><th colspan="2">Inputs</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	Inputs		Output	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1	$X = A \text{ OR } B$ (logic notation) $X = A + B$ (Boolean algebra)
Inputs		Output																		
A	B	X																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	1																		

10.2.4 NAND gate (NOT AND)



▲ Figure 10.5

Description:	Truth table:	How to write this:
The output, X, is 1 if: input A AND input B are NOT both 1	▼ Table 10.5	X = A NAND B (logic notation) X = $\overline{A \cdot B}$ (Boolean algebra)

10.2.5 NOR gate (NOT OR)



▲ Figure 10.6

Description:	Truth table:	How to write this:																		
The output, X, is 1 if: neither input A nor input B is 1	▼ Table 10.6	X = A NOR B (logic notation) X = $\overline{A + B}$ (Boolean algebra)																		
	<table><tr><th colspan="2">Inputs</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>		Inputs		Output	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
	Inputs		Output																	
	A		B	X																
	0		0	1																
	0		1	0																
	1		0	0																
1	1	0																		

10.2.6 XOR gate



▲ Figure 10.7

Description:	Truth table:	How to write this:																		
<p>The output, X, is 1 if:</p> <p>(input A is 1 AND input B is 0)</p> <p>or</p> <p>(input A is 0 AND input B is 1)</p>	▼ Table 10.7	X = A XOR B (logic notation)																		
	<table><tr><th colspan="2">Inputs</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	Inputs		Output	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0	X = (A . \overline{B}) + (\overline{A} . B) (Boolean algebra)
	Inputs		Output																	
	A	B	X																	
	0	0	0																	
	0	1	1																	
	1	0	1																	
1	1	0																		
		NOTE: this is sometimes written as: (A + B) . ($\overline{A \cdot B}$)																		

Activity 10.1

Show why $X = (A \text{ AND NOT } B) \text{ OR } (\text{NOT } A \text{ AND } B)$
and
 $Y = (A \text{ OR } B) \text{ AND } (\text{NOT } (A \text{ AND } B))$ both represent the same logic gate.